

Deliverables for the Final Project

FRA Function Settings: (Frequency Response Analysis)

- 1Vpp Amplitude
- High-Z
- 10Hz – 10kHz
- At least 60 Points (The more points the better, it will take longer)
- Correct Channels for Vin (Source) Vout (Output)

Specification	Requirement	Proof of Requirement (Deliverable in Report)
Speaker Resistance	8 Ohms	Nothing, its given to you
Bass Filter -3dB cut-off (Lowpass Filter)	<p>320Hz \pm10%</p> <p>(Cut off needs to be in the range of 288Hz – 352Hz)</p> <p>(Shows that your Bass Filter will filter at the right frequency)</p> <p>(Make sure to isolate the filter)</p>	<p>Use FRA function on Oscilloscope. (Look at settings above)</p> <p>2 Probes (Vin, Vout)</p> <p>A plot of Phase and Magnitude of the filter with a cursor or marker on the -3dB cut off point.</p>
Mid Filter with two -3dB cut-offs (Midpass Filter)	<p>320Hz \pm10% to 3200Hz \pm10%</p> <p>(Lower cut off needs to be in the range of 288Hz – 352Hz)</p> <p>(Higher cut off needs to be in the range of 2880Hz – 3520Hz)</p> <p>(Shows that your Mid Filter will filter at the right frequency)</p> <p>(Make sure to isolate the filter)</p>	<p>Use FRA function on Oscilloscope. (Look at settings above)</p> <p>2 Probes (Vin, Vout)</p> <p>A plot of Phase and Magnitude of the filter with a cursor on the lower -3dB cut off point.</p> <p>A plot of Phase and Magnitude of the filter with a cursor on the higher -3dB cut off point.</p>
Treble Filter with -3dB cut-off (Highpass Filter)	<p>3200Hz \pm10%</p> <p>(Cut off needs to be in the range of 2880Hz – 3520Hz)</p> <p>(Shows that your Treble Filter will filter at the right frequency)</p> <p>(Make sure to isolate the filter)</p>	<p>Use FRA function on Oscilloscope. (Look at settings above)</p> <p>2 Probes (Vin, Vout)</p> <p>A plot of Phase and Magnitude of the filter with a cursor or</p>

		marker on the -3dB cut off point.
Vamp with all equalizer knobs turned to minimum settings.	<p>Vamp < 15mVrms at 200Hz, 2kHz, 10kHz</p> <p>(Shows that your equalizer has minimal leakage voltage on low, mid and high frequencies, when the volume is the lowest)</p> <p>(Make sure to turn all knobs to the lowest position)</p>	<p>3 Screenshots:</p> <p>2 Probes (Vin, Vout)</p> <p>Vin = 1Vpp @ 200Hz Show that: Vamp < 15mVrms</p> <p>Vin = 1Vpp @ 2000Hz Show that: Vamp < 15mVrms</p> <p>Vin = 1Vpp @ 10000Hz Show that: Vamp < 15mVrms</p>
Vamp with all equalizer knobs turned to maximum settings.	<p>Vamp = 100 mVrms \pm 10% at 200Hz, 2kHz, 10kHz (90Vrms < Vamp < 110Vrms)</p> <p>(Shows that your equalizer has the correct gain low, mid and high frequencies)</p> <p>(Make sure to turn all knobs to the highest position)</p>	<p>3 Screenshots:</p> <p>2 Probes (Vin, Vamp)</p> <p>Vin = 1Vpp @ 200Hz Show that: 90Vrms < Vamp < 110Vrms</p> <p>Vin = 1Vpp @ 2000Hz Show that: 90Vrms < Vamp < 110Vrms</p> <p>Vin = 1Vpp @ 10000Hz Show that: 90Vrms < Vamp < 110Vrms</p>
Vamp,max – Vamp,min max ripple with equalizer at max	<p>15mVrms from 200Hz to 10kHz</p> <p>(Shows that your equalizer frequency response is a straight line)</p> <p>(Make sure to turn all knobs to the highest position)</p>	<p>Use FRA function on Oscilloscope. (Look at settings above)</p> <p>2 Probes (Vin, Vamp)</p> <p>A plot of Phase and Magnitude of the equalizer with a cursor on the maximum magnitude.</p> <p>A plot of Phase and Magnitude of the equalizer with a cursor on the minimum magnitude.</p> <p>A handwritten calculation showing that the difference in</p>

		voltage of the maximum and minimum is less than 15mVrms.
Amplifier Output Power	<p>Pamp > 400mW from 200Hz to 10kHz</p> <p>(Shows that your amplifier is amplifying correctly at all frequencies)</p> <p>(Make sure to turn all knobs to the highest position)</p>	<p>Use FRA function on Oscilloscope. (Look at settings above)</p> <p>2 Probes (Vin, Vspeaker)</p> <p>A plot of Phase and Magnitude of the whole design with a cursor on the minimum magnitude.</p> <p>A picture of the amount of current the amp is drawing from the Power Supply when your design is playing music.</p> <p>A handwritten calculation showing that at the minimum magnitude the power is above 400mW</p>